The circuit diagram shows a current source $K_a i_a$ (pointing up), a resistor $\frac{1}{D}$ with current $D\omega$ flowing down, and a capacitor J with voltage ω (+ on top, − on bottom) and current $J\frac{d\omega}{dt}$ flowing down.